

FLIP-FLOP

Aim:- Truth table verification of Flip-Flops:

RS FLIP-FLOP

- (i) JK Master Slave
- (ii) D- Type
- (iii) T- Type.

Apparatus Required:-

IC 7410, IC 7400, etc.



Procedure:-

1. Connections are made as per circuit diagram.
2. The truth table is verified for various combinations of inputs.



Truth Table:- (Master Slave JK Flip-Flop)

Preset	Clear	J	K	Clock	Q_{n+1}	$\overline{Q_{n+1}}$	
0	1	X	X	X	1	0	Set
1	0	X	X	X	0	1	Reset
1	1	0	0	\square	Q_n	$\overline{Q_n}$	No Change
1	1	0	1	\square	0	1	Reset
1	1	1	0	\square	1	0	Set
1	1	1	1	\square	$\overline{Q_n}$	Q_n	Toggle

D Flip-Flop:-

Preset	Clear	D	Clock	Q_{n+1}	$\overline{Q_{n+1}}$
1	1	0		0	1
1	1	1		1	0

T Flip-Flop:-

Preset	Clear	T	Clock	Q_{n+1}	$\overline{Q_{n+1}}$
1	1	0		Q_n	$\overline{Q_n}$
1	1	1		$\overline{Q_n}$	Q_n

Exercise:-

- Write the timing diagrams for all the above Flip-Flops


Pin Details: -

CK1	1	16	K1
PR1	2	15	Q1
Clr1	3	14	Q1'
J1	4	13	Gnd
VCC	5	12	K2
CK2	6	11	Q2
PR2	7	10	Q2'
Clr2	8	9	J2

Truth Table:-

Clock	QC	QB	QA
0	0	0	0
1	0	0	1
2	0	1	0
3	0	1	1
4	1	0	0
5	1	0	1
6	1	1	0
7	1	1	1

Timing Diagram:-

 

Preset	Clear	J	K	Clock	Q_{n+1}	$\overline{Q_{n+1}}$	
0	1	X	X	X	1	0	Set
1	0	X	X	X	0	1	Reset
1	1	0	0	\square	Q_n	$\overline{Q_n}$	No Change
1	1	0	1	\square	0	1	Reset
1	1	1	0	\square	1	0	Set
1	1	1	1	\square	$\overline{Q_n}$	Q_n	Toggle

(a) Connect the two NOR gates as shown in Figure 1.

 


Figure 1. An RS Flip-Flop created using NOR gates.

(b) Vary the inputs R and S (i.e. 0 and +5V) to obtain all the possible combinations for Q and /Q.

(c) In your opinion why is there a Q and /Q output? In your opinion how does this circuit work?

Section 2. The Synchronous Flip-Flop

(a) Synchronous means that this flip-flop is concerned with time! Digital circuits can have a concept of time using a clock signal. The clock signal simply goes from low-to-high and high-to-low in a short period of time.

 


Figure 2. A typical clock signal.

 


Figure 3. The Synchronous Flip Flop.

Implement the circuit in Figure 3. You can simulate a clock signal by moving the clock line from low to high and back again to low.

(b) Vary inputs R and S and apply the clock pulse. Write the output states into a table as below:

Q_n/Q_{n+1}	R	S	Q_{n+1}/Q_{n+1}	Q_{n+1}
0	1	0	0	
1	0	0	0	
0	1	0	1	
1	0	0	1	
0	1	1	0	
1	0	1	0	
0	1	1	1	
1	0	1	1	

(c) Convert the circuit into a D-type flip flop (as shown in Figure 4.)

 


Figure 4. The D-type flip-flop

Draw up the truth table for a D-type flip flop. In your opinion how does it work? what could this circuit be useful for?