

MUX/DEMUX USING 74153 & 74139

Aim: - To verify the truth table of multiplexer using 74153 & to verify a demultiplexer using 74139. To study the arithmetic circuits half-adder half Subtractor, full adder and full Subtractor using multiplexer.


Apparatus Required: -

IC 74153, IC 74139, IC 7404, etc.

Procedure: - (IC 74153)

1. The Pin [16] is connected to + Vcc.
2. Pin [8] is connected to ground.
3. The inputs are applied either to 'A' input or 'B' input.
4. If MUX 'A' has to be initialized, E_a is made low and if MUX 'B' has to be initialized, E_b is made low.
5. Based on the selection lines one of the inputs will be selected at the output and thus the truth table is verified.
6. In case of half adder using MUX, sum and carry is obtained by applying a constant inputs at I_{0a} , I_{1a} , I_{2a} , I_{3a} and I_{0b} , I_{1b} , I_{2b} and I_{3b} and the corresponding values of select lines are changed as per table and the
7. In this case, the channels A and B are kept at constant inputs according to the table and the inputs A and B are varied. Making E_a and E_b zero and the output is taken at Z_a , and Z_b .
8. In full adder using MUX, the input is applied at C_{n-1} , A_n and B_n . According to the table corresponding outputs are taken at C_n and D_n .


MULTIPLEXERS

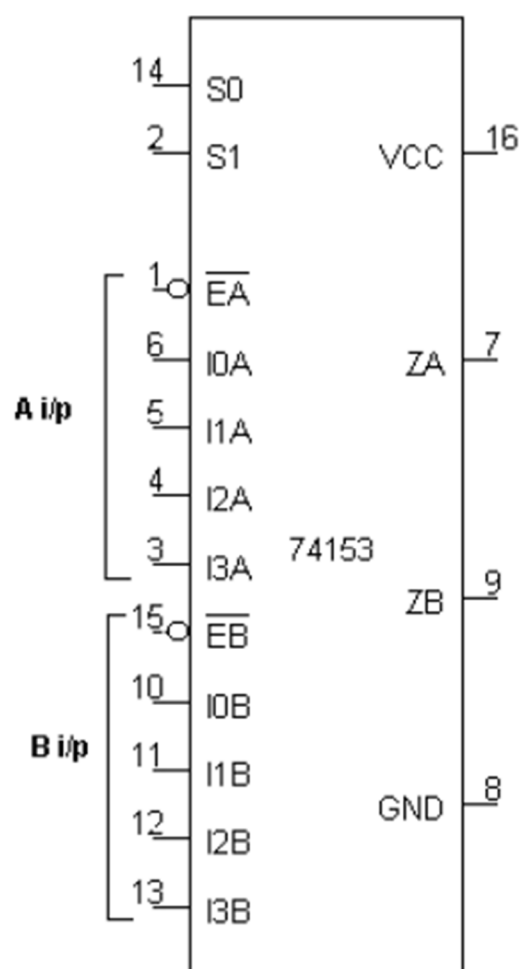

CHANNEL – A							
INPUTS					SELECT LINES		O/P
E _a	I _{0a}	I _{1a}	I _{2a}	I _{3a}	S1	S2	Z _a (v)
1	X	X	X	X	X	X	0
0	0	X	X	X	0	0	0
0	1	X	X	X	0	0	1
0	X	0	X	X	0	1	0
0	X	1	X	X	0	1	1
0	X	X	0	X	1	0	0
0	X	X	1	X	1	0	1
0	X	X	X	0	1	1	0
0	X	X	X	1	1	1	1

CHANNEL – B							
INPUTS					SELECT LINES		O/P
E _a	I _{0b}	I _{1b}	I _{2b}	I _{3b}	S1	S2	Z _a (v)
1	X	X	X	X	X	X	0
0	0	X	X	X	0	0	0
0	1	X	X	X	0	0	1
0	X	0	X	X	0	1	0
0	X	1	X	X	0	1	1
0	X	X	0	X	1	0	0
0	X	X	1	X	1	0	1
0	X	X	X	0	1	1	0
0	X	X	X	1	1	1	1

DUAL 2 TO 4 LINE DEMULTIPLEXERS

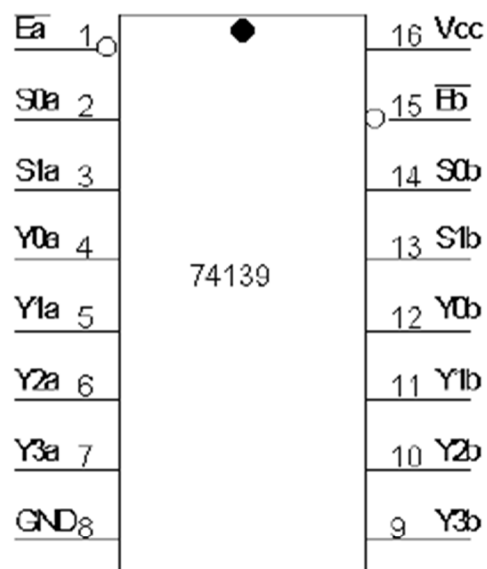


Truth Table For Demux: -


CHANNEL – A						
Inputs			Outputs			
$\bar{E}a$	$S1a$	$S0a$	$Y0a$	$Y1a$	$Y2a$	$Y3a$
1	X	X	1	1	1	1
0	0	0	0	1	1	1
0	0	1	1	0	1	1
0	1	0	1	1	0	1
0	1	1	1	1	1	0

CHANNEL – B						
Inputs			Outputs			
$\bar{E}b$	$S1b$	$S0b$	$Y0b$	$Y1b$	$Y2b$	$Y3b$
1	X	X	1	1	1	1
0	0	0	0	1	1	1
0	0	1	1	0	1	1
0	1	0	1	1	0	1
0	1	1	1	1	1	0

Full Adder Using 74153: -

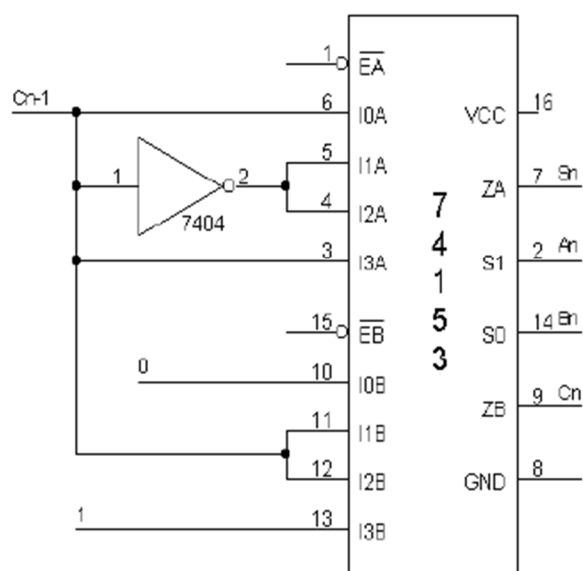


Full Subtractor Using 74153: -

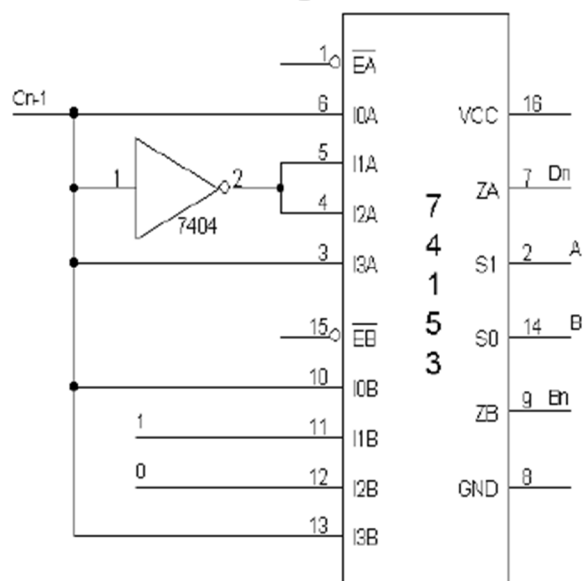

Truth Tables: - Same for both Subtractor and adder


Half adder/subtractor				Full Adder/subtractro				
A	B	Sn/Dn (V)	Cn/Bn (V)	An	Bn	Cn-1	Sn/Dn (V)	Cn/Bn (V)
0	0			0	0	0		
0	1			0	0	1		
1	0			0	1	0		
1	1			0	1	1		
0	0			1	0	0		
0	1			1	0	1		
1	0			1	1	0		
1	1			1	1	1		

Half adder

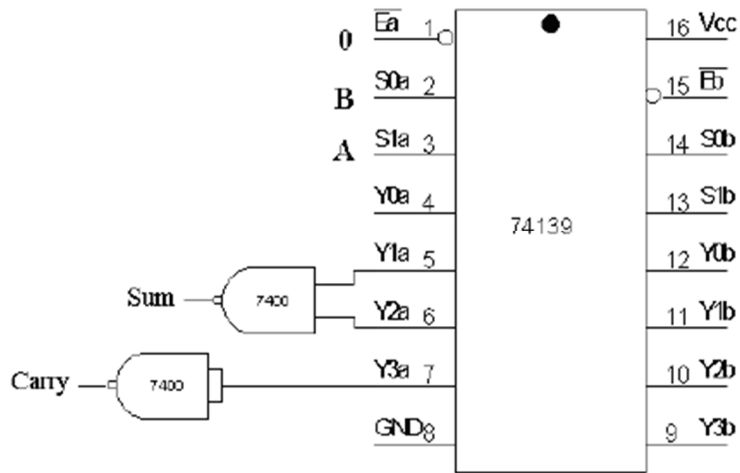

Half Adder			
A	B	Sn (V)	Cn (V)
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

Half subtractor:-

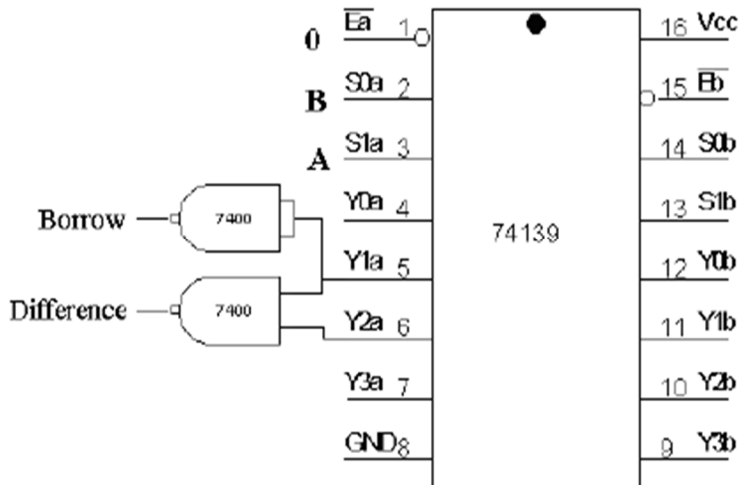

Half Subtractor			
A	B	Dn (V)	Bn (V)
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0